

**Abdalrahman Ali Eltaher**

**Group 2**

**Assignment\_1**

## • Q[1]

### ➤ Code:


```
Q1.v
E: > Deploma karem > [not_extra]Assignmen_1 > Q1.v
1 module Q_1(A,B,C,D,E,F,out,out_bar,sel);
2 input A,B,C,D,E,F,sel ;
3 output out,out_bar ;
4 wire z1,z2;
5 assign z1=A & B & C;
6 assign z2 = D ^ E ^ F;
7 assign out = (sel == 1)? z2 : z1;
8 assign out_bar = (sel == 1)? ~z2 : ~z1;
9
10 endmodule
```

### ➤ Wave:

:: A = 1 , B = 0 and C = 1 ∴ z1 = 0

:: D = 1 , E = 0 and F = 0 ∴ z2 = 0

:: sel = 1 ∴ out = 0 and out\_bar = 1

 


Q[2]

➤ Code:

```
exercise.v  Q2.v  Settings
E: > Diploma karem > [not_extra]Assignmen_1 > Q2.v
1  module Q_2(A,B,C,sel,D,out,out_bar);
2  input[2:0] D;
3  input A,B,C,sel;
4  output reg out,out_bar ;
5  reg out_AND,out_OR,out_XNOR ;
6  always @(*) begin
7      out_AND = D[0] & D[1];
8      out_OR = D [2] | out_AND ;
9      out_XNOR = ~ (A ^ B ^ C ) ;
10     if (sel == 1) begin
11         out = out_XNOR ;
12         out_bar = ~out_XNOR;
13     end
14     else begin
15         out = out_OR ;
16         out_bar = ~ out_OR;
17     end
18
19 end
20
21 endmodule
```

➤ Wave:

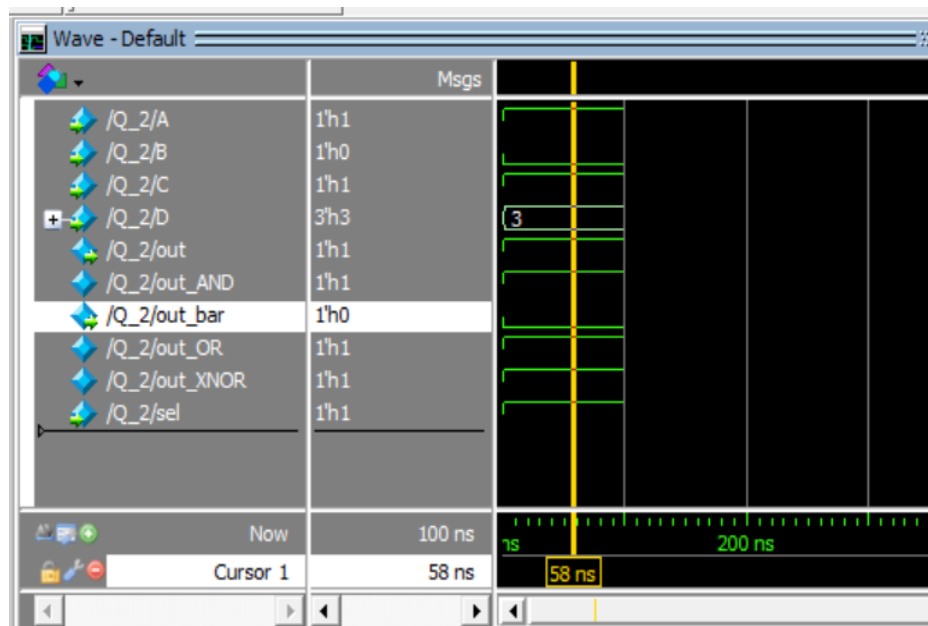- The input D is 3'b011 and The input A=1,B=0 and C =1.  
∴ out\_AND = 1 ,out\_OR =1 and out\_XNOR =1  
∵ sel =1 ∴ out = out\_XNOR =1 and out\_bar = not out\_XNOR =0



- Q[3]


➤ Code:

```


oma karem > [not_extra]Assignmen_1 > Q3.v
module x4bit_adder(A,B,C,carry);
input [3:0] A,B;
output [3:0] C ;
output carry ;
assign {carry,C} = A + B ;
endmodule

```

➤ Wave:

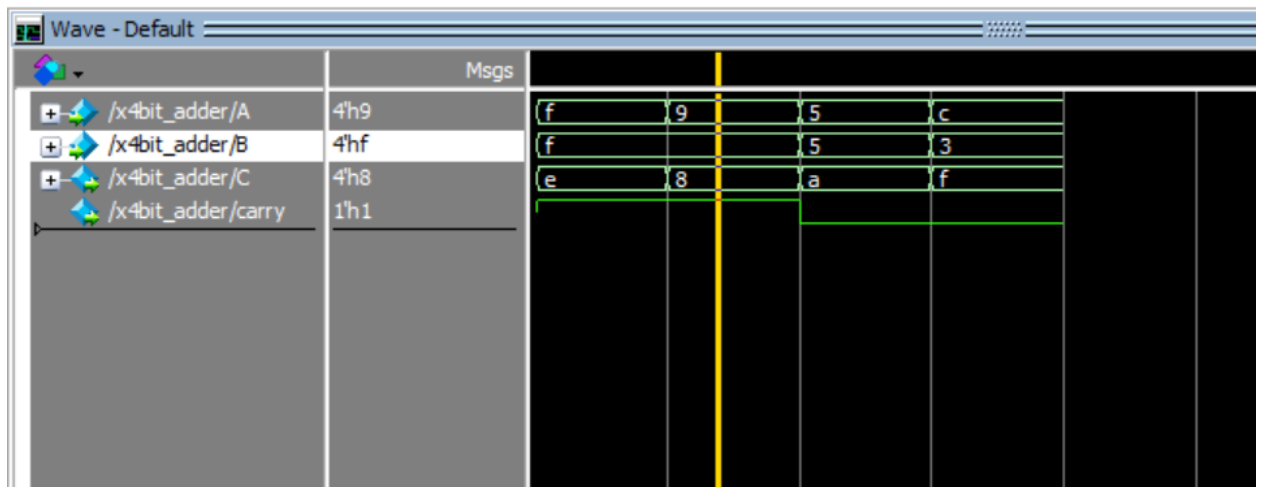

➤ Schematic:

 

- Q[4]


- Code:

```
1 module decoder_2x4(A,D);  
2 input [1:0]A ;  
3 output [3:0]D;  
4 assign D = (A == 2'b00)? 4'b0001 : (A == 2'b01)? 4'b0010 : (A == 2'b10)? 4'b0100 : 4'b1000 ;  
5 endmodule
```

- Wave:

Wave - Default						
		Msgs				
+	/decoder_2x4/A	2'h0	3	2	1	0
	/decoder_2x4/D	4'h1	8	4	2	1

- Schematic:

 


## • Q[5]

### ➤ Code:

```
E: > Deploma karem > [not_extra]Assignmen_1 > Q5.v
1 module even_parity(A, out_with_parity);
2 input[7:0] A ;
3 output [8:0] out_with_parity ;
4 wire parity_bit;
5 assign parity_bit = ^ A;
6 assign out_with_parity ={A,parity_bit};
7 endmodule
```
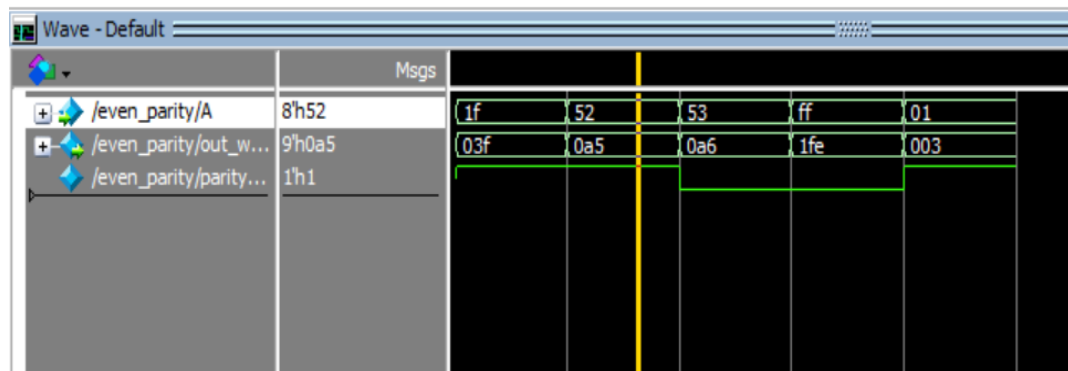
### ➤ Wave:

- Even Parity If number of 1s is even, parity bit value is 0. If number of 1s is odd, parity bit value is 1.



## • Q[6]

➤ Code:

```

1 module seven_segment(A,B,opcode,Result,a,b,c,d,e,f,g,enable);
2 parameter N =4 ;
3 input [N-1:0] A ,B ;
4 input [N-3:0] opcode ;
5 input enable ;
6 output reg [N-1:0] Result ;
7 output reg a,b,c,d,e,f,g;
8 always @(*) begin
9     // ALU operation
10    case (opcode)
11        2'b00: Result = A + B ;
12        2'b01: Result = A | B ;
13        2'b10: Result = A - B ;
14        2'b11: Result = A ^ B ;
15    endcase
16    // 7_segment
17    if (enable == 1'b1) begin
18        case ( Result)
19            4'b0000:begin a=1'b1;b= 1'b1;c=1'b1;d=1'b1;e=1'b1;f=1'b1;g=1'b0;end
20            4'b0001:begin a=1'b0;b= 1'b1;c=1'b1;d=1'b0;e=1'b0;f=1'b0;g=1'b0;end
21            4'b0010:begin a=1'b1;b= 1'b1;c=1'b0;d=1'b1;e=1'b1;f=1'b0;g=1'b1;end
22            4'b0011:begin a=1'b1;b= 1'b1;c=1'b1;d=1'b1;e=1'b0;f=1'b0;g=1'b1;end
23            4'b0100:begin a=1'b0;b= 1'b1;c=1'b1;d=1'b0;e=1'b0;f=1'b1;g=1'b1;end
24            4'b0101:begin a=1'b1;b= 1'b0;c=1'b1;d=1'b1;e=1'b0;f=1'b1;g=1'b1;end
25            4'b0110:begin a=1'b1;b= 1'b0;c=1'b1;d=1'b1;e=1'b1;f=1'b1;g=1'b1;end
26            4'b0111:begin a=1'b1;b= 1'b1;c=1'b1;d=1'b0;e=1'b0;f=1'b0;g=1'b0;end
27            4'b1000:begin a=1'b1;b= 1'b1;c=1'b1;d=1'b1;e=1'b1;f=1'b1;g=1'b1;end
28            4'b1001:begin a=1'b1;b= 1'b1;c=1'b1;d=1'b1;e=1'b0;f=1'b1;g=1'b1;end
29            4'b1010:begin a=1'b1;b= 1'b1;c=1'b1;d=1'b0;e=1'b1;f=1'b1;g=1'b1;end
30            4'b1011:begin a=1'b0;b= 1'b0;c=1'b1;d=1'b1;e=1'b1;f=1'b1;g=1'b1;end
31            4'b1100:begin a=1'b1;b= 1'b0;c=1'b0;d=1'b1;e=1'b1;g=1'b1;end
32            4'b1101:begin a=1'b0;b= 1'b1;c=1'b1;d=1'b1;e=1'b1;f=1'b0;g=1'b1;end
33            4'b1110:begin a=1'b1;b= 1'b0;c=1'b0;d=1'b1;e=1'b1;f=1'b1;g=1'b1;end
34            4'b1111:begin a=1'b1;b= 1'b0;c=1'b0;d=1'b0;e=1'b1;f=1'b1;g=1'b1;end
35        endcase
36    end
37    else begin
38        a=1'b0;b= 1'b0;c=1'b0;d=1'b0;e=1'b0;f=1'b0;g=1'b0;
39    end
40 end
41 endmodule

```

➤ Wave:

